

Homework#1 Solutions

Problem 1: Use DeMorgan's Law to write an expression for F' where

- a) $F(x, y, z) = x(y' + z)$
- b) $F(x, y, z) = xy + x'z + yz'$
- c) $F(w, x, y, z) = xyz'(y'z + x)' + (w'yz + x')$

Solution: a) $F(x, y, z) = x(y' + z)$

$$F' = (x(y' + z))' = x' + (y' + z)' = x' + yz'$$

b) $F(x, y, z) = xy + x'z + yz'$

$$F' = (xy + x'z + yz')' = (xy)'(x'z)'(yz')' = (x' + y')(x + z')(y' + z)$$

c) $F(w, x, y, z) = xyz'(y'z + x)' + (w'yz + x')$

$$F' = (xyz'(y'z + x)' + (w'yz + x'))'$$

$$F' = (xyz'(y'z)'x' + (w'yz + x'))'$$

$$F' = (w'yz)'(x')' = (w + y' + z')x$$

Problem 2: Functions F , G , and H are defined in the following way:

$$F = A'C' + A'B'C$$

$$G = A'B' + A'C'$$

$$H = A'B'C' + A'C' + B'C$$

Which of the functions are equivalent?

Solution:

A	B	C	F	G	H
0	0	0	1	1	1
0	0	1	1	1	1
0	1	0	1	1	1
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	0	1
1	1	0	0	0	0
1	1	1	0	0	0

Functions F and G are equivalent.

By Algebra:

$$F = A'C' + A'B'C$$

$$? = A'B' + A'C' = G$$

$$F = A'C' + A'B'C$$

$$? = A'B'(C + C') + A'C' = G$$

$$F = A'C' + A'B'C$$

$$? = A'B'C + A'B'C' + A'C' = G$$

$$F = A'C' + A'B'C$$

$$? = A'B'C + A'C'(B' + 1) = G$$

$$F = A'C' + A'B'C$$

$$== A'B'C + A'C' = G$$

$$H = A'B'C' + A'C' + B'C$$

$$? = A'C' + A'B'C = F$$

$$H = A'C'(B + 1) + (A' + A)B'C$$

$$? = A'C' + A'B'C = F$$

$$H = A'C' + A'B'C + AB'C$$

$$!= A'C' + A'B'C = F$$

Can not simplify anymore. To ensure that, you can't simplify anymore, the best way is to write out each side to minterms or maxterms and compare minterms.

Problem 3: For each of the following functions:

$$J = ((A' + B)' + C')' + DC' + AB'$$

$$K = x(y + w'z) + (w' + x' + z')'$$

- Create the truth table for each expression.
- Name the minterms ($\Sigma m(?)$) and maxterms ($\Pi M(?)$) for each expression.
- Simplify each expression using boolean logic.**
- Draw a 2-level gate network (AND-OR or OR-AND) for the expression in c), whichever form uses the fewest gates. DO NOT SIMPLIFY the expression first.
- How many literals in each expression from (c)? How many terms in the expression from (c)?**
- Draw 2-level gate networks for the simplified expressions in NAND-NAND or NOR-NOR form.
- Write the Boolean expressions for the complement of each expression (eg. J') in product of sums form. DO NOT SIMPLIFY.

Solution:

A	B	C	D	J
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

b) Minterms: $J(A,B,C,D) = \Sigma m(1, 2, 3, 5, 6, 7, 8, 9, 10, 11, 13, 14, 15)$

Maxterms: $J(A,B,C,D) = \Pi M(0, 4, 12)$

c) $J = (A + B + C + D)(A + B' + C + D)(A' + B' + C + D)$

$J = (A + B + C + D)(A + B' + C + D)(A + B' + C + D)(A' + B' + C + D)$

$J = ((B + B')(A + C + D))((A + A')(B' + C + D))$



$J = (A + C + D)(B' + C + D)$

~~d)~~

e) J has 6 literals and 2 terms.

f)

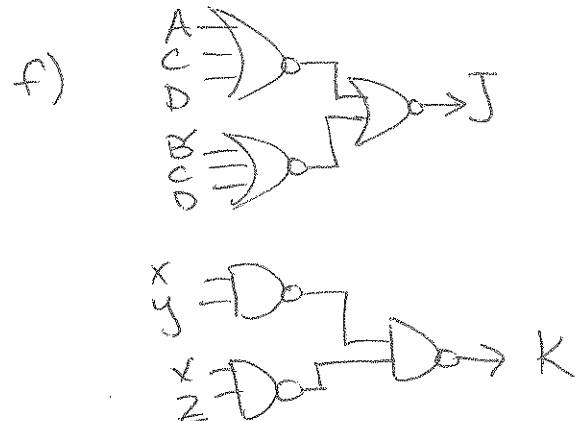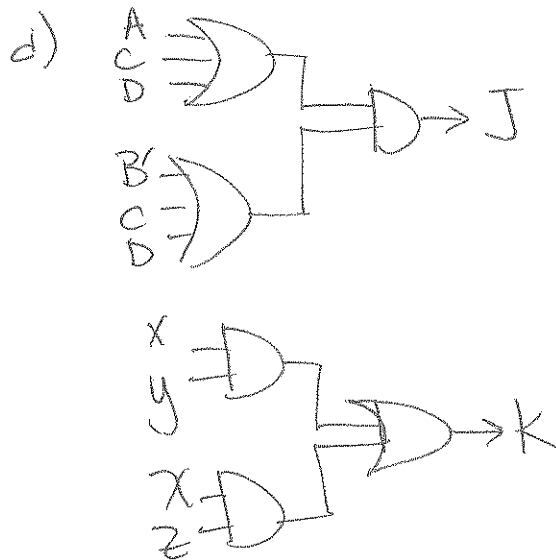g) $J'(A, B, C, D) = A'B'C'D' + A'BC'D' + ABC'D'$



	w	x	y	z	K
	0	0	0	0	0
	0	0	0	1	0
	0	0	1	0	0
	0	0	1	1	0
	0	1	0	0	0
	0	1	0	1	1
	0	1	1	0	1
a)	0	1	1	1	1
	1	0	0	0	0
	1	0	0	1	0
	1	0	1	0	0
	1	0	1	1	0
	1	1	0	0	0
	1	1	0	1	1
	1	1	1	0	1
	1	1	1	1	1

b) Minterms: $K(w,x,y,z) = \sum m(5, 6, 7, 13, 14, 15)$

Maxterms: $K(w,x,y,z) = \prod M(0, 1, 2, 3, 4, 8, 9, 10, 11, 12)$

c) $K = x(y + w'z) + (w' + x' + z)'$

$$K = xy + w'xz + wxz$$

$$K = xy + (w' + w)xz$$

$$K = xy + xz$$

d) See above

e) K has 4 literals and 2 terms.

g) $K'(w, x, y, z) = (w + x' + y + z')(w + x' + y' + z)(w + x' + y + z')(w' + x' + y + z')(w' + x' + y' + z)(w' + x' + y' + z')$

Problem 4: For each of the following functions:

x	y	z	P	Q
0	0	0	0	1
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	0	1
1	0	1	1	1
1	1	0	1	1
1	1	1	1	0

- Name the minterms ($\Sigma m(?)$) and maxterms ($\Pi M(?)$) for P and Q.
- Draw a 2-level gate network (AND-OR or OR-AND). Do NOT simplify the expression first.
- Write the minterm and maxterm expression in boolean logic.
- Simplify each expression from (c) using boolean logic.
- Draw 2-level gate networks for the simplified expressions in NAND-NAND or NOR-NOR form.
- Write the Boolean expressions for the complement of each P and Q (ie. P' and Q') in product of sums form. DO NOT SIMPLIFY.


Solution:

a)

$$P(x,y,z) = \Sigma m(1, 5, 6, 7) \quad P(x,y,z) = \Pi M(0, 2, 3, 4)$$

$$Q(x,y,z) = \Sigma m = (0, 1, 4, 5, 6) \quad Q(x,y,z) = \Pi M = (2, 3, 7)$$

b)

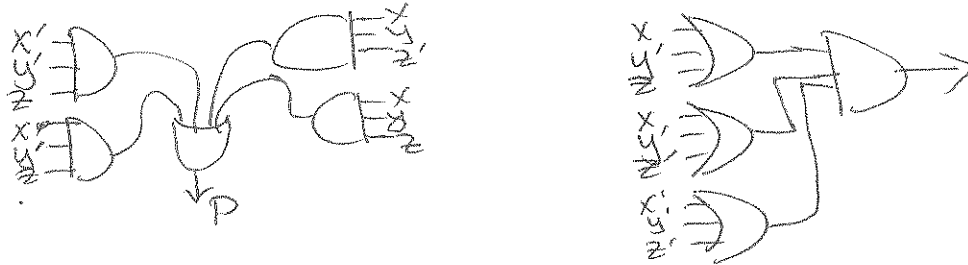

c)

$$\text{minterm: } P = x'y'z + xy'z + xyz' + xyz$$

$$Q = x'y'z' + x'y'z + xy'z' + xy'z + xyz'$$

$$\text{maxterm: } P = (x + y + z)(x + y' + z)(x + y' + z')(x' + y + z)$$

$$Q = (x + y' + z)(x + y' + z')(x' + y' + z')$$

d)

$$P = x'y'z + xy'z + xyz' + xyz$$

$$P = (x' + x)y'z + xy(z + z')$$

$$P = y'z + xy$$

$$Q = x'y'z' + x'y'z + xy'z' + xy'z + xyz'$$

$$Q = x'y'z' + x'y'z + xy'z + xy'z'(1 + 1) + xyz'$$



$$Q = (x'y'z' + x'y'z + xy'z + xy'z') + (xyz' + xy'z')$$

$$Q = y'(x'z' + x'z + xz' + xz) + xz'(y + y')$$

$$Q = y'(x + x')(z + z') + xz'$$

$$Q = y' + xz'$$

e)

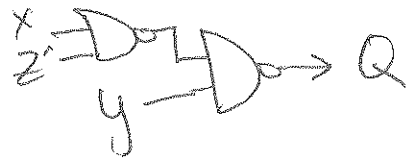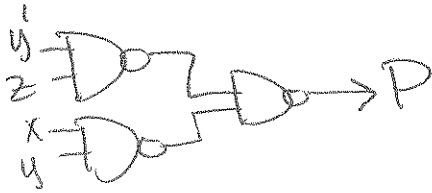



f)

$$P' = (x + y + z')(x' + y + z')(x' + y' + z)(x' + y' + z')$$

$$Q' = (x + y + z)(x + y + z')(x' + y + z)(x' + y + z')(x' + y' + z)$$



d)

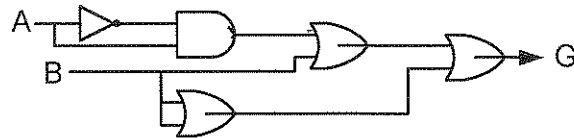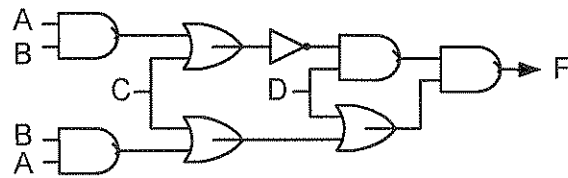Problem 5: For the following diagrams, give boolean expressions. Simplify and redraw the system.




Solution:

Circuit Function:

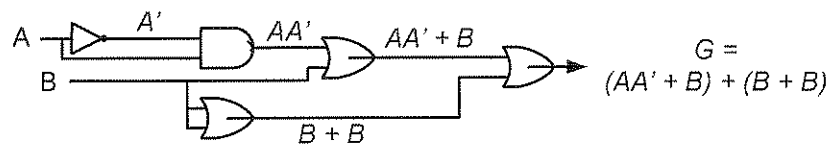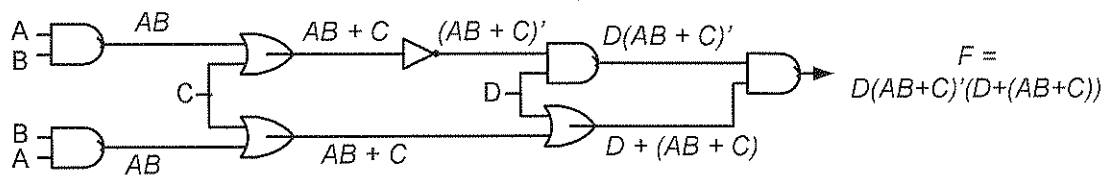

Simplified Circuits:

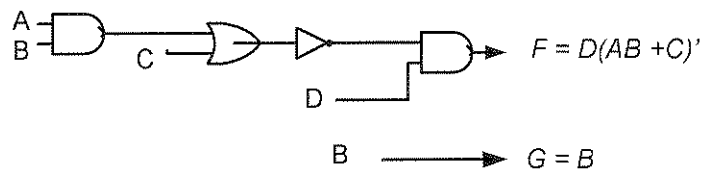

Problem 6: Convert the following truth table to a switching expression (Boolean Algebra) and simplify the expression as much as possible.

x	y	z	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Solution:

x	y	z	F	minterm
0	0	0	1	$x'y'z'$
0	0	1	1	$x'y'z$
0	1	0	1	$x'yz'$
0	1	1	0	
1	0	0	0	
1	0	1	1	$xy'z$
1	1	0	0	
1	1	1	0	

$$F = x'y'z' + x'y'z + x'yz' + xy'z$$

$$F = x'z'(y' + y) + y'z(x' + x)$$

$$F = x'z' + y'z$$

Problem 7: Using the postulates of Boolean algebra, prove the following formulae:

a) $x'y'z' + x'y'z + x'yz + xy'z + xyz = x'y' + z$

b) $ABC' + A'C'D + AB'C' + BC'D + A'D = AC' + A'D$

c) $wxy + w'xy + x'(zw + zy') + z(x'w' + y'x) = xy + z$

Solution:

a) $x'y'z' + x'y'z + x'yz + xy'z + xyz = x'y' + z$

$$x'y'z' + x'y'z(1 + 1) + x'yz + xy'z + xyz = x'y' + z$$

$$x'y'z' + x'y'z + x'y'z + x'yz + xy'z + xyz = x'y' + z$$

$$x'y'(z' + z) + z(x'y' + x'y + xy' + xy) = x'y' + z$$

$$x'y' + z((x + x')y' + (x + x')y) = x'y' + z$$

$$x'y' + z(y' + y) = x'y' + z$$

$$x'y' + z = x'y' + z$$

b) $ABC' + A'C'D + AB'C' + BC'D + A'D = AC' + A'D$

$$\begin{aligned}
ABC' + A'C'D + AB'C' + BC'D + A'D &= AC' + A'D \\
ABC' + AB'C' + BC'D + A'D(C + C') &= AC' + A'D \\
ABC' + AB'C' + BC'D + A'D &= AC' + A'D \\
AC'(B + B') + BC'D + A'D &= AC' + A'D \\
AC' + BC'D(A + A') + A'D &= AC' + A'D \\
AC' + ABC'D + A'BC'D + A'D &= AC' + A'D \\
AC'(1 + BD) + A'D(1 + BC') &= AC' + A'D \\
AC' + A'D &= AC' + A'D
\end{aligned}$$

c) $wxy + w'xy + x'(zw + zy') + z(x'w' + y'x) = xy + z$

$$\begin{aligned}
(w + w')xy + x'(zw + zy') + z(x'w' + y'x) &= xy + z \\
xy + z(x'w + x'y') + z(x'w' + y'x) &= xy + z \\
xy + z(x'w + x'y' + x'w' + y'x) &= xy + z \\
xy + z(x'(w + w') + y'(x + x')) &= xy + z \\
xy + z(x' + y') &= xy + z \\
xy + z(xy)' &= xy + z \\
xy(1 + z) + z(xy)' &= xy + z \\
xy + xyz + z(xy)' &= xy + z \\
xy + z(xy + (xy)') &= xy + z \\
xy + z &= xy + z
\end{aligned}$$