


Homework #3

Quiz in Lecture on Thurs 10/2/14 - No Make-up Quizzes!



- Calculate the Critical path through each of your gate networks for the previous problems and the ones below given the following delays.

Gate	Timing
AND	3ns
OR	4ns
NOT	1ns
NAND	2ns
NOR	2ns

Gate	Timing
XOR	2ns
Multiplexor (any size)	3ns
Decoder	5ns
Encoder	4ns

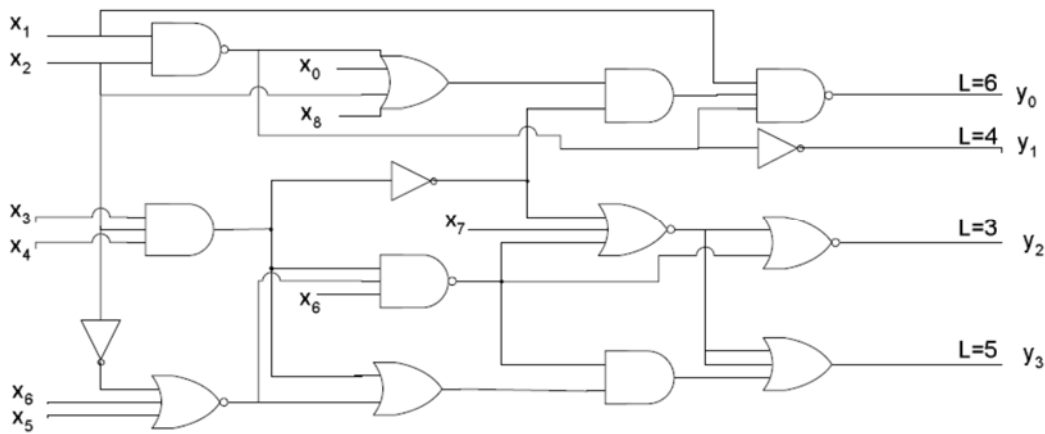


(ignore L numbers in figure)

  

- Design a black box that converts a decimal digit (0-9) in binary as (X_3, X_2, X_1, X_0) to its 4-bit Excess-3 encoding (Z_3, Z_2, Z_1, Z_0) (<http://en.wikipedia.org/wiki/Excess-3>). [From Wikipedia] In Excess-3, numbers are represented as decimal digits, and each digit is represented by four bits as the digit value + 3 (the "excess" amount). Eg. 7 becomes 10, 9 becomes 12.
 - Complete the truth table: input (X_3, X_2, X_1, X_0) , output (Z_3, Z_2, Z_1, Z_0)
 - Write the minterm expressions for each output.
 - Implement all Z outputs with a single 4-bit Decoder and OR gates.
- Design a black box that has a 4-bit input (X) and a 4-bit output (Y) which computes $Y = (9x) \% 16$. Use only a decoder and an encoder.
 - Create the truth table with decimal values.

 
- b. Draw a Decoder. (How many inputs/outputs does it have? How does it work?)
 - c. Draw an Encoder. (How many inputs/outputs does it have? How does it work?)
 - d. Connect the Decoder to the Encoder according to the truth table in (a). Make sure to label all input and output values.
4. Design a 2-bit adder with Carry_in and Carry_out signals from logic gates.
 - a. Create the truth table and Boolean logic expressions for 2-bit SUM and Carry_out signals.
 - b. Implement (a) using basic logic gates (AND, OR NOT, NAND, NOR, or MUX).
 - c. Implement (a) using 1-bit full adders.
5. Using 2-bit adders from the previous problem, construct a 8-bit adder.
6. Using 2-bit (1-selector) multiplexors and 1-bit Adders, build a 2-bit ALU as described by the figure (with Carryout and zero output signals) which performs the following functions. Numbers are in two's complement form. Note: There is no Carry_in signal.



c ₁	c ₀	Operation
0	0	Negate B
0	1	A-B
1	0	A+B
1	1	A XOR B

 
7. Implement a 1-bit ALU with inputs and outputs as shown in the figure. The ALU must perform the operations shown in the table according to the specified control signals. Use one MUX gate and NOR gates to implement the unit. Assume only uncomplemented forms of the variables are given.

SLTZ stands for “set on less than zero”. If A is < 0 , then output 1, otherwise output 0.



C ₁	C ₀	Operation
0	0	A + B + Carry_in
0	1	SLT
1	0	B - A
1	1	SLTZ

 8. Implement a 1-bit ALU with inputs and outputs as shown in the figure. The ALU must perform the operations shown in the table according to the specified control signals. Use AND, OR, NOT and MUX gates to implement the unit. Assume only uncomplemented forms of the variables are given.



C_2	C_1	C_0	Operation
0	0	0	$A' \text{ AND } B'$
0	0	1	$A \text{ NOR } B$
0	1	0	$A \text{ XOR } B$
0	1	1	$A \text{ NAND } B$
1	0	0	$A+B$ (carryout)
1	0	1	$A - B$
1	1	0	B'
1	1	1	SLT (if $B < A$, result = 1, else result = 0)

9. Consider two new gates \square and \odot described by the following truth table. Write the minimal Boolean expression for the gate. Show that each gate is a universal gate by building another universal set of gates. You may use the constants 0 and 1 if needed.

x	y	$x \square y$	$x \odot y$
0	0	0	1
0	1	1	0
1	0	0	1
1	1	0	1