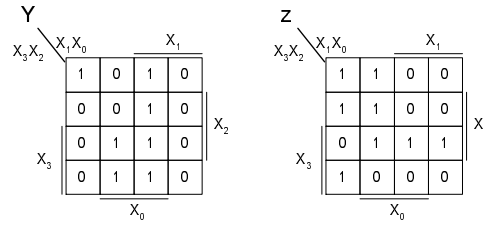



# CS320 Fall 2014

## Homework#2 Solutions

**Problem 1:** Find the minimal sum of products and products of sums for the functions shown in the k-maps. Implement Y using a NAND-NAND network, and implement Z using NOR-NOR network.



**Solution:**

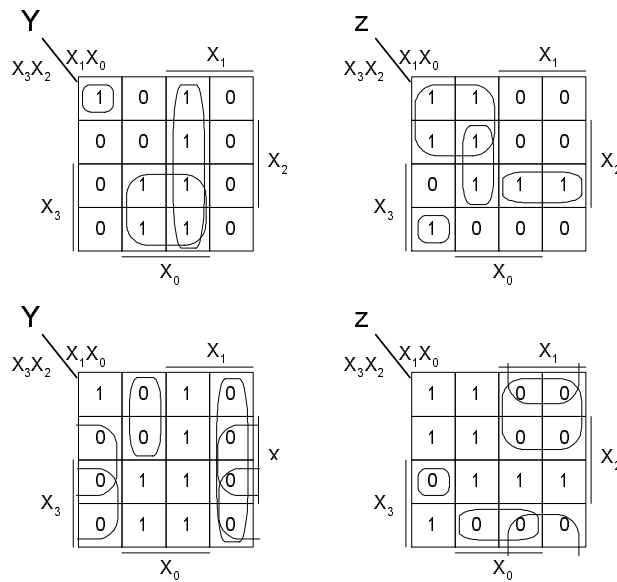


NAND-NAND for Y: Sum of products

$$Y = x'_3x'_2x'_1x'_0 + x_3x_0 + x_1x_0$$

NOR-NOR for X: Product of sums
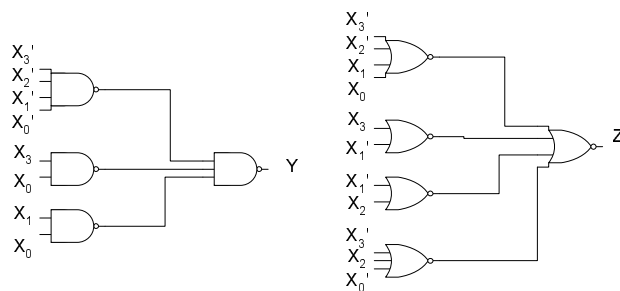
$$Z = (x'_3 + x'_2 + x_1 + x_0)(x_3 + x'_1)(x_2 + x'_1)(x'_3 + x_2 + x'_0)$$




**Problem 2:** A logic circuit realizes the function  $F(a,b,c,d) = a'b' + a'cd + ac'd + ab'd'$ . Assuming that  $a=c$  never occurs when  $b = d = 1$ , find a simplified expression and circuit for  $F$ . (Hint: When can Don't-Cares be used?)

**Solution:**


Begin by creating a table of the function  $F$ , and then determining the Don't cares ( $F'$ ). This step can be skipped, if one can go straight to k-maps.

a	b	c	d	F	F'
0	0	0	0	1	1
0	0	0	1	1	1
0	0	1	0	1	1
0	0	1	1	1	1
0	1	0	0	0	0
0	1	0	1	0	-
0	1	1	0	0	0
0	1	1	1	1	1
1	0	0	0	1	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	0	0
1	1	0	0	0	0
1	1	0	1	1	1
1	1	1	0	0	0
1	1	1	1	0	-

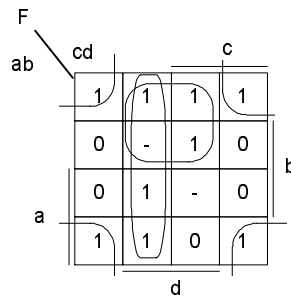

$$F' = b'd' + c'd + a'd$$

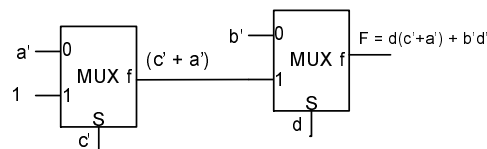One implementation of this Function using 2-input Muxes:



**Problem 3:** Design a black box that has a 3-bit input  $x$ , and a 3-bit output  $y$ . The function of the unit is  $y = (5x) \% 8$ . Create the truth table and implement with the minimal gate logic in NAND-NAND and NOR-NOR for each output.

**Solution:**

Decimal x	(5x) mod 8 y	$x_2$	$x_1$	$x_0$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	0
1	5	0	0	1	1	0	1
2	2	0	1	0	0	1	0
3	7	0	1	1	1	1	1
4	4	1	0	0	1	0	0
5	1	1	0	1	0	0	1
6	6	1	1	0	1	1	0
7	3	1	1	1	0	1	1

From the K-maps shown below we obtain:


Minterms and maxterms require same number of gates for  $y_2$

$$y_2 = x_2'x_0 + x_2x_0'$$

$$y_2 = (x_2 + x_0)(x_2' + x_0')$$

$$y_1 = x_1$$

$$y_0 = x_0$$

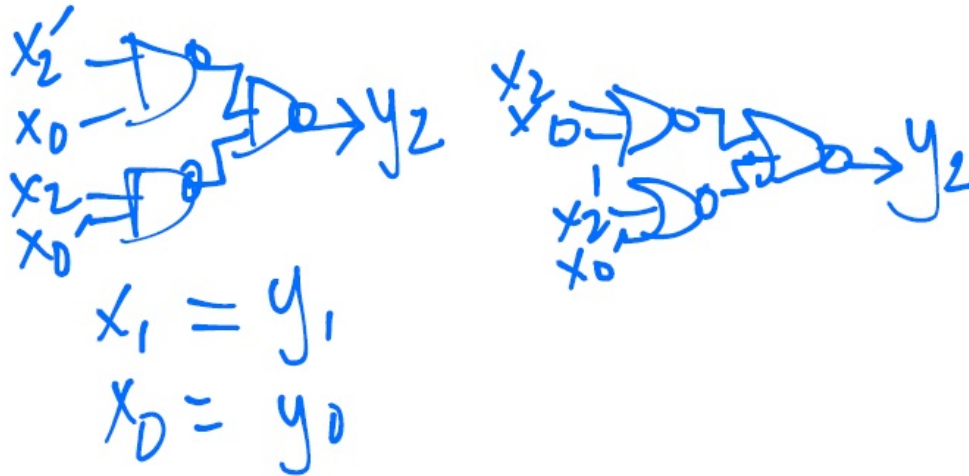

**Problem 4:** Design a system that takes a two digit base 3 number as input and produces the corresponding binary value (Z). (Example input:  $12_3 = 0101_2$ ). Create the truth table and implement the 2 most significant bits using the minimal number of 2-input multiplexors (selector is 1-bit).

**Solution:**

Since the largest value of the input  $22_3 = 8_{10}$ , we need 3 bits to represent output.

$a_1$	$a_0$	$b_1$	$b_0$	$y_3$	$y_2$	$y_1$	$y_0$
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	-	-	-	-
0	1	0	0	0	0	1	1
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	1
0	1	1	1	-	-	-	-
1	0	0	0	0	1	1	0
1	0	0	1	0	1	1	1
1	0	1	0	1	0	0	0
1	0	1	1	-	-	-	-
1	1	0	0	-	-	-	-
1	1	0	1	-	-	-	-
1	1	1	0	-	-	-	-
1	1	1	1	-	-	-	-

From the K-maps shown below we obtain:

$$y_3 = a_1b_1$$


$$y_2 = a_1\bar{b}_1 + a_0b_1 + a_0b_0 = (a_1\bar{b}_1 + a_0b_1) + a_0b_0$$

$$y_1 = a_1\bar{b}_1 + a_0\bar{b}_1\bar{b}_0 + a_1\bar{a}_0b_1$$

$$= (a_1 + a_0\bar{b}_0)\bar{b}_1 + a_1\bar{a}_0b_1$$

$$y_0 = a_1b_0 + \bar{a}_0b_0 + a_0\bar{b}_0 = (a_1 + \bar{a}_0)b_0 + a_0\bar{b}_0$$

**Problem 5:** Given two inputs  $x = (x_1, x_0)$  and  $y = (y_1, y_0)$ , the output is the absolute value of their difference:  $z = |2y - x|$ . Use multiplexers to implement the function.

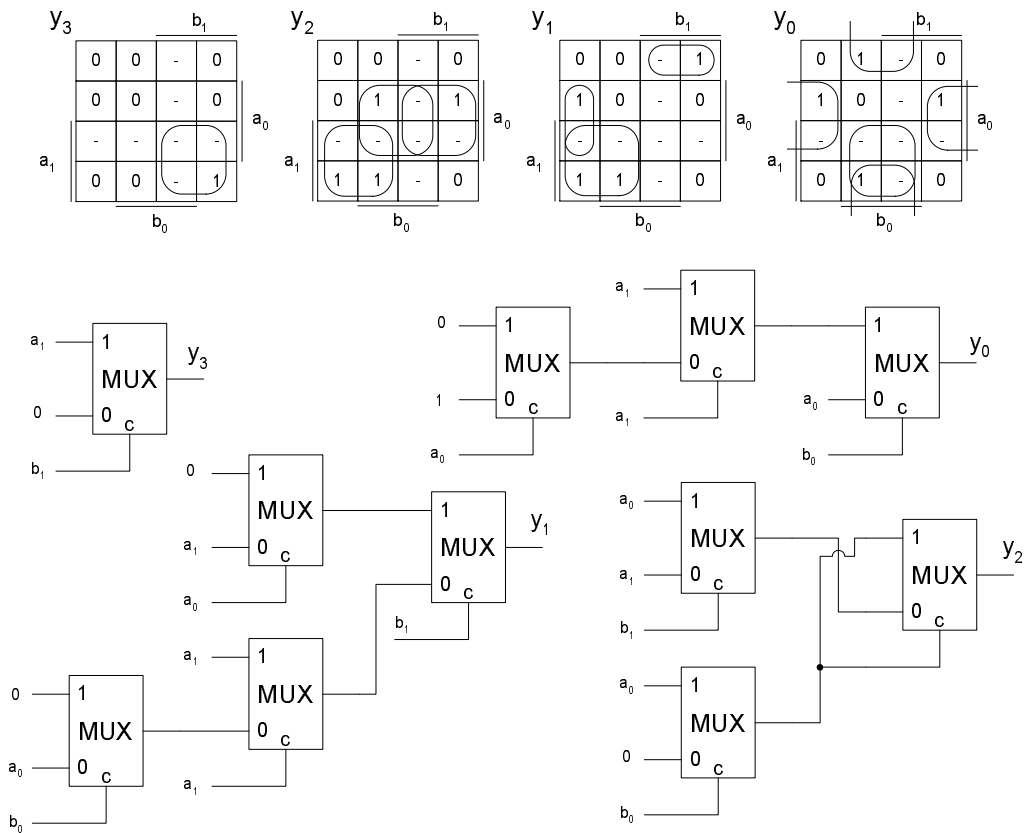

**Solution:**

Largest number for Y is 3, and smallest x is 0, therefore  $|2 * 3 - 0| = 6$ . The represent 6 we need at least 3 bits.


$x_1$	$x_0$	$y_1$	$y_0$	Z (decimal)	$Z_2$	$Z_1$	$Z_0$
0	0	0	0	0	0	0	0
0	0	0	1	2	0	1	0
0	0	1	0	4	1	0	0
0	0	1	1	6	1	1	0
0	1	0	0	1	0	0	1
0	1	0	1	1	0	0	1
0	1	1	0	3	0	1	1
0	1	1	1	5	1	0	1
1	0	0	0	2	0	1	0
1	0	0	1	0	0	0	0
1	0	1	0	2	0	1	0
1	0	1	1	4	1	0	0
1	1	0	0	3	0	1	1
1	1	0	1	1	0	0	1
1	1	1	0	1	0	0	1
1	1	1	1	3	0	1	1

$$Z_2 = x'_0 y_1 y_0 + x'_1 y_1 y_0 + x'_1 x'_0 y_1$$

$$Z_1 = x'_1 x'_0 y_0 + x_1 y'_1 y'_0 + x_1 x_0 y_1 y_0 + x'_1 x_0 y_1 y'_0 + x_1 x'_0 y_1 y'_0$$


$$Z_0 = x_0$$

$Z_2$  :

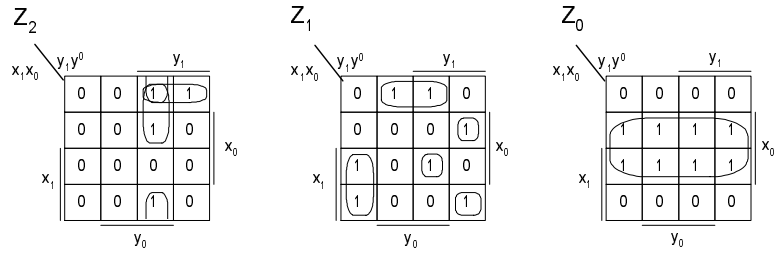

$$\begin{aligned}
 & x'_0 y_1 y_0 + x'_1 y_1 y_0 + x'_1 x'_0 y_1 \\
 & x_0 (x'_1 y_1 y_0) + x'_0 (y_1 y_0 + x'_1 y_1) \\
 & x'_1 y_1 y_0 \Rightarrow x_1 (1) + x'_1 (y_1 y_0) \\
 & y_1 y_0 + x'_1 y_1 \Rightarrow x_1 (y_1 y_0) + x'_1 (y_1 + y_1 y_0) = x_1 (y_1 y_0) + x'_1 (y_1) \\
 & Z_1 :
 \end{aligned}$$
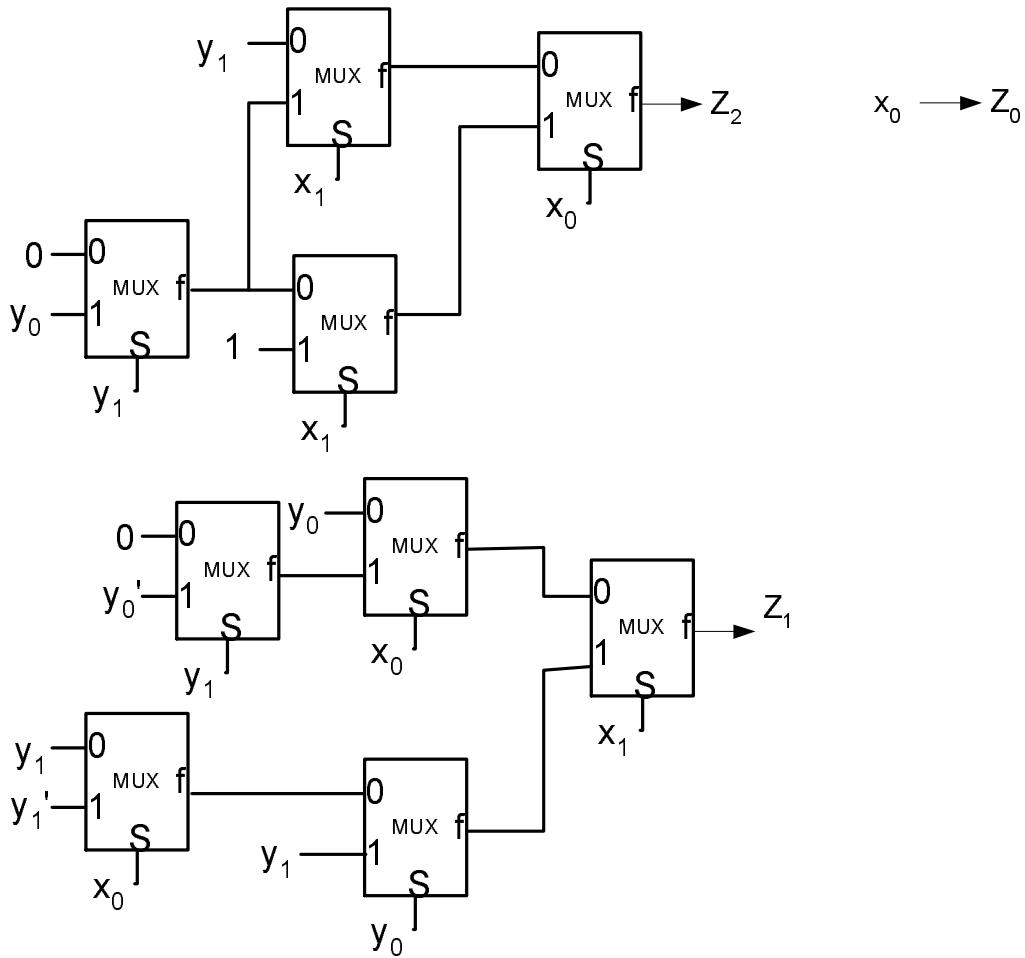
$$\begin{aligned}
 & x'_1 x'_0 y_0 + x_1 y'_1 y'_0 + x_1 x_0 y_1 y_0 + x'_1 x_0 y_1 y'_0 + x_1 x'_0 y_1 y'_0 \\
 & x_1 (x_0 y'_1 y'_0 + y_1 y_0 + x'_0 y_1 y'_0) + x'_1 (x'_0 y_0 + x_0 y_1 y'_0) \\
 & x_0 y'_1 y'_0 + y_1 y_0 + x'_0 y_1 y'_0 \Rightarrow y_0 (y_1) + y'_0 (x_0 y'_1 + x'_0 y_1) \\
 & x_0 y'_1 + x'_0 y_1 \Rightarrow x_0 (y'_1) + x'_0 (y_1)
 \end{aligned}$$



**Problem 6:** A circuit will either subtract X from Y or Y from X, depending on the value of A. If A = 1, the output should be  $|X - Y|$ , and if A = 0, the output should be  $|Y - X|$ . Design a combinational system for the output using as few multiplexers as possible.

**Solution:**

A	$X_1$	$X_0$	$Y_1$	$Y_0$	$ X - Y $ or $ Y - X $	$Z_1$	$Z_0$
0	0	0	0	0	0	0	0
0	0	0	0	1	1	0	1
0	0	0	1	0	2	1	0
0	0	0	1	1	3	1	1
0	0	1	0	0	1	1	0
0	0	1	0	1	0	0	0
0	0	1	1	0	1	0	1
0	0	1	1	1	2	1	0
0	1	0	0	0	1	0	1
0	1	0	0	1	1	0	1
0	1	0	1	0	0	0	0
0	1	0	1	1	1	0	1
0	1	1	0	0	3	1	1
0	1	1	0	1	2	1	0
0	1	1	1	0	1	0	1
0	1	1	1	1	0	0	0
1	0	0	0	0	0	0	0
1	0	0	0	1	1	0	1
1	0	0	1	0	2	1	0
1	0	0	1	1	3	1	1
1	0	1	0	0	1	0	1
1	0	1	0	1	0	0	0
1	0	1	1	0	1	0	1
1	0	1	1	1	2	1	0
1	1	0	0	0	2	1	0
1	1	0	0	1	1	0	1
1	1	0	1	0	0	0	0
1	1	0	1	1	1	0	1
1	1	1	0	0	3	1	1
1	1	1	0	1	2	1	0
1	1	1	1	0	1	0	1
1	1	1	1	1	0	0	0

The output is the same whether or not A is 1 or 0. For this reason, the output is not dependant on A. Therefore, we can disregard A in the rest of the design.

$$z_1 = x_1x_0y'_1 + x'_1y_1y_0 + x'_1x'_0y_1 + y'_1y'_0x_0$$

$$z_0 = x_1y'_1y_0 + x_0y_1y'_0 + x'_0y_0$$


$z_1 :$

$$x_1(x_0y'_1) + x'_1(y_1y_0 + x'_0y_1)$$


$$y_1y_0 + x'_0y_1 \Rightarrow y_1(y_0 + x'_0) + y'_1(0)$$

$z_0 :$

$$y_0(x_1y'_1 + x'_0) + y'_0(x_0y_1)$$

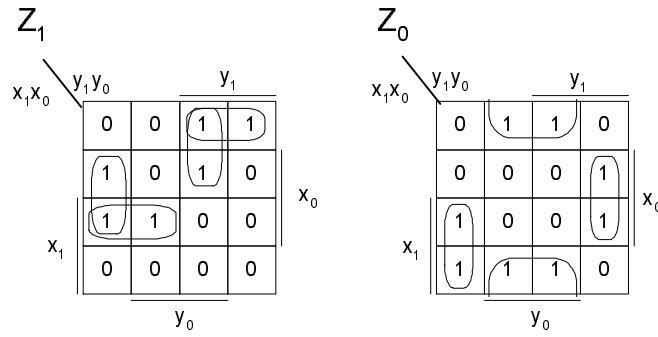

$$x_1 y_1' + x_0' \Rightarrow x_0'(1) + x_0(x_1 y_1')$$

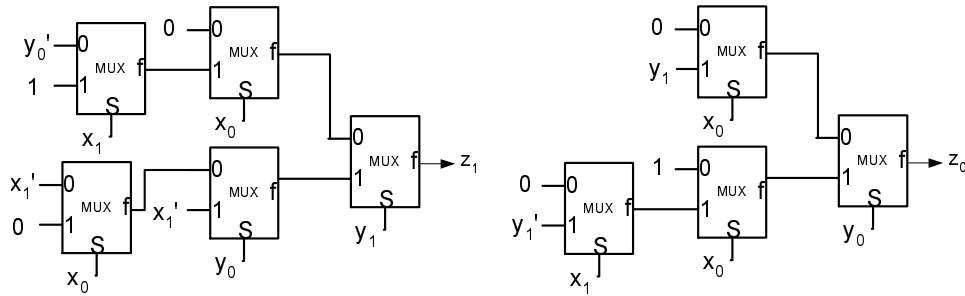


**Problem 7:** Implement the following expression using multiplexers (Only uncomplemented variables are given.):  $f = x_1'x_2' + x_3'x_2x_1' + x_1x_2'$

**Solution:**

$$f = x_2'(x_1' + x_1) + x_3'x_2x_1'$$

$$f = x_2' + x_3'x_2x_1'$$

$$f = x_2'(1) + x_2(x_3'x_1')$$

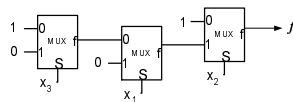

**Problem 8:** Implement the following function using (a) an 8-input multiplexor (3-selector), (b) a 4-input multiplexor (2-selector) and NOR gates

$$Z = a'b'c'd + a'bc'd' + a'b'cd + ab'c'd + abcd + abcd'$$

**Solution:**

(a):

Select 3 variables to be the selector variables: abc

$$Z = a'b'c'(d) + a'b'c(d) + a'bc'(d') + a'bc(d) + ab'c'(d) + ab'c(d) + abc'(0) + abc(d + d')$$


(b):

Select 2 variables to be the selector variables: ab


$$Z = a'b'(c'd + cd) + a'b(c'd') + ab'(c'd) + ab(cd + cd')$$

$$Z = a'b'(c'd + cd) + a'b(c'd') + ab'(c'd) + ab(c)(d + d')$$
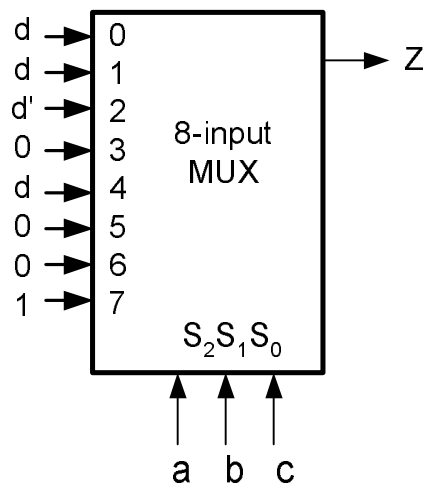
$$Z = a'b'(c'd + cd) + a'b(c'd') + ab'(c'd) + ab(c)$$



(a)

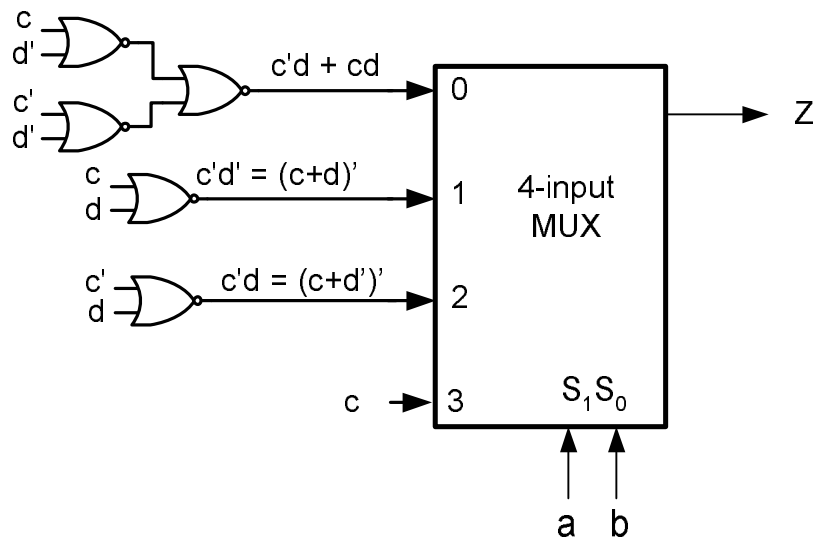

(b)